

Timing and Verification

Design of Digital Circuits 2017

Srdjan Capkun

Onur Mutlu

(Guest starring: Frank K. Gürkaynak and Aanjan Ranganathan)

http://www.syssec.ethz.ch/education/Digitaltechnik_17

What will we learn

■ Timing in Combinational circuits

- Propagation and Contamination Delays

■ Timing for Sequential circuits

- Setup and Hold time
- How fast can my circuit work?

■ How timing is modeled in Verilog

■ Verification using Verilog

- How can we make sure the circuit works correctly
- Designing Testbenches

The Goal Of Circuit Design Is To Optimize:

■ Area

- Net circuit area is proportional to the cost of the device

■ Speed / Throughput

- We want circuits that work faster, or do more


■ Power / Energy

- Mobile devices need to work with a limited power supply
- High performance devices dissipate more than $100\text{W}/\text{cm}^2$

■ Design Time


- Designers are expensive
- The competition will not wait for you

Requirements Depend On Application

 


Timing

 - Until now, we investigated mainly functionality
- What determines how fast a circuit is and how can we make faster circuits?



Propagation and Contamination Delay

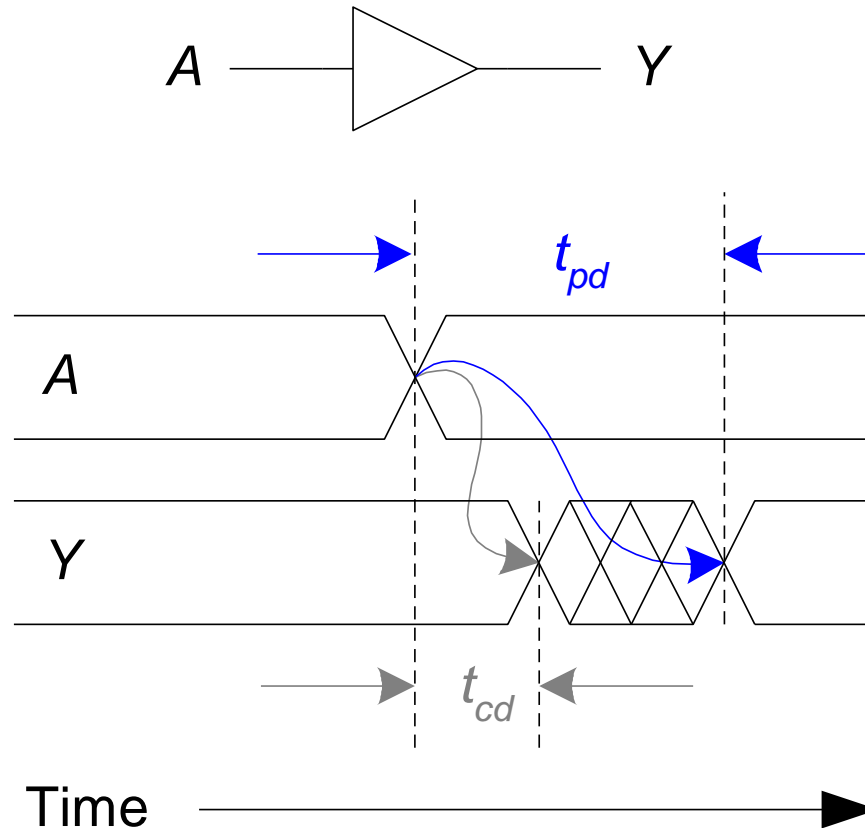- **Propagation delay:** t_{pd} = max delay from input to output
- **Contamination delay:** t_{cd} = min delay from input to output



Propagation & Contamination Delay


■ Delay is caused by

- Capacitance and resistance in a circuit
- Speed of light limitation (not as fast as you think!)

■ Reasons why t_{pd} and t_{cd} may be different:

- Different rising and falling delays
- Multiple inputs and outputs, some of which are faster than others
- Circuits slow down when hot and speed up when cold

Critical (Long) and Short Paths

 

■ Critical (Long) Path:

$$t_{pd} = 2 t_{pd_AND} + t_{pd_OR}$$

■ Short Path:


$$t_{cd} = t_{cd_AND}$$

Propagation times

Table 2.7 Timing specifications for multiplexer circuit elements


Gate	t_{pd} (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

Propagation times

 

$$\begin{aligned}
 t_{pd_sy} &= t_{pd_INV} + t_{pd_AND3} + t_{pd_OR4} \\
 &= 30 \text{ ps} + 80 \text{ ps} + 90 \text{ ps} \\
 &= 200 \text{ ps}
 \end{aligned}$$

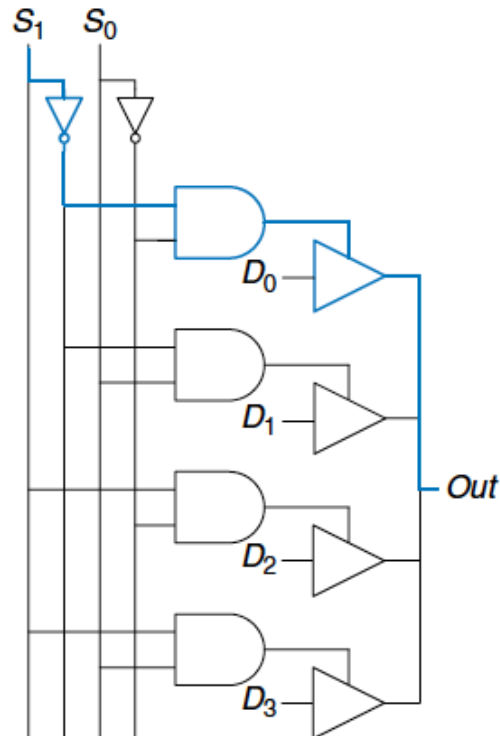(a) $t_{pd_dy} = t_{pd_AND3} + t_{pd_OR4}$
 $= 170 \text{ ps}$



$$\begin{aligned}
 t_{pd_sy} &= t_{pd_INV} + t_{pd_AND2} + t_{pd_TRI_SY} \\
 &= 30 \text{ ps} + 60 \text{ ps} + 35 \text{ ps} \\
 &= 125 \text{ ps}
 \end{aligned}$$


(b) $t_{pd_dy} = t_{pd_TRI_AY}$
 $= 50 \text{ ps}$

Figure 2.73 4:1 multiplexer propagation delays:
 (a) two-level logic,
 (b) tristate

Sequential Timing


- Flip-flop samples D at clock edge
- D must be stable when it is sampled
- Similar to a photograph, D must be stable around the clock edge
- If D is changing when it is sampled, *metastability* can occur
 - Recall that a flip-flop copies the input D to the output Q on the rising edge of the clock. This process is called sampling D on the clock edge. If D is stable at either 0 or 1 when the clock rises, this behavior is clearly defined. But what happens if D is changing at the same time the clock rises?

D Flip-Flop Symbols

 


Input Timing Constraints

 - **Setup time:** t_{setup} = time before the clock edge that data must be stable (i.e. not changing)
- **Hold time:** t_{hold} = time after the clock edge that data must be stable
- **Aperture time:** t_a = time around clock edge that data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)




Output Timing Constraints

 - **Propagation delay:** t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- **Contamination delay:** t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)




Dynamic Discipline

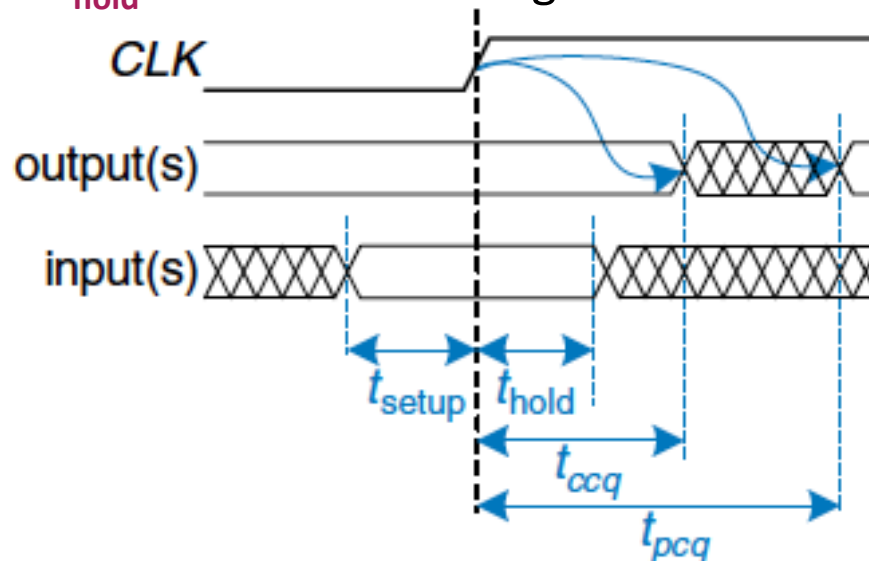- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge



Dynamic Discipline

 - The delay between registers has a minimum and maximum delay, dependent on the delays of the circuit elements




Setup Time Constraint

- The clock period or cycle time, T_c , is the time between rising edges of a repetitive clock signal. Its reciprocal, $f_c=1/T_c$, is the clock frequency.
- All else being the same, increasing the clock frequency increases the work that a digital system can accomplish per unit time.
- Frequency is measured in units of Hertz (Hz), or cycles per second:
 - 1 megahertz (MHz) 10^6 Hz
 - 1 gigahertz (GHz) 10^9 Hz.

Setup Time Constraint

 
- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

Setup Time Constraint

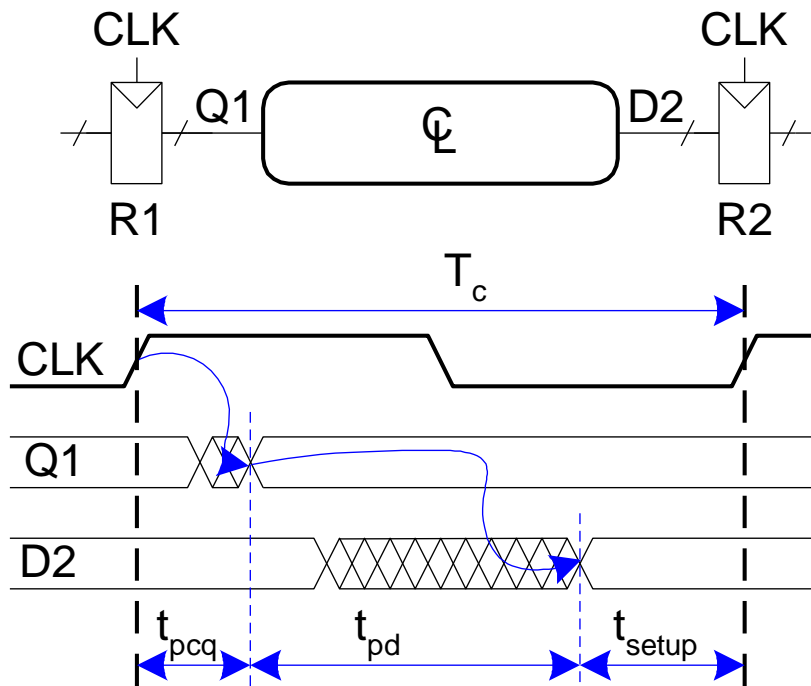- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.




$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$

$$t_{\text{pd}} \leq$$

Setup Time Constraint

 - The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

Hold Time Constraint

 
- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$t_{\text{hold}} <$

Hold Time Constraint

 
- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} >$$


Hold Time Constraint

 - The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

Timing Analysis

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c = 1/T_c =$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$


per gate

$$\begin{cases} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{cases}$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate $\begin{bmatrix} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{bmatrix}$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

(30 + 25) ps > 70 ps ? No!

Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c =$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$


per gate $\begin{bmatrix} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{bmatrix}$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \begin{cases} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{cases}$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$

Clock Skew

 - The clock doesn't arrive at all registers at the same time
- Skew is the difference between two clock edges
- Examine the worst case to guarantee that the dynamic discipline is not violated for any register – many registers in a system!



Preikestolen - Norway



Stay away from both **HOLD** and **SETUP** !



How Do You Know That A Circuit Works?

- **You have written the Verilog code of a circuit**
 - Does it work correctly?
 - Even if the syntax is correct, it might do what you want?
 - What exactly it is that you want anyway?
- **Trial and error can be costly**
 - You need to 'test' your circuit in advance
- **In modern digital designs, functional verification is the most time consuming design stage.**

The Idea Behind A Testbench

- **Using a computer simulator to test your circuit**
 - You instantiate your design
 - Supply the circuit with some inputs
 - See what it does
 - Does it return the “correct” outputs?

Testbenches

- HDL code written to test another HDL module, the *device under test* (dut), also called the *unit under test* (uut)
- Not synthesizable
- Types of testbenches:
 - Simple testbench
 - Self-checking testbench
 - Self-checking testbench with testvectors

Example

- Write Verilog code to implement the following function in hardware:

$$y = (\overline{b} \cdot \overline{c}) + (a \cdot \overline{b})$$

- Name the module sillyfunction

Example

- Write Verilog code to implement the following function in hardware:

$$y = (\overline{b} \cdot \overline{c}) + (a \cdot \overline{b})$$

- Name the module sillyfunction

```
module sillyfunction(input  a, b, c,  
                    output y);  
  
    assign y = ~b & ~c | a & ~b;  
endmodule
```

Simple Testbench

```
module testbench1(); // Testbench has no inputs, outputs
    reg  a, b, c;      // Will be assigned in initial block
    wire y;

    // instantiate device under test
    sillyfunction dut (.a(a), .b(b), .c(c), .y(y) );d

    // apply inputs one at a time
    initial begin          // sequential block
        a = 0; b = 0; c = 0; #10; // apply inputs, wait 10ns
        c = 1; #10;           // apply inputs, wait 10ns
        b = 1; c = 0; #10;    // etc .. etc..
        c = 1; #10;
        a = 1; b = 0; c = 0; #10;
    end
endmodule
```

Simple Testbench

- Simple testbench instantiates the design under test
- It applies a series of inputs
- The outputs have to be observed and compared using a simulator program.
 - This type of testbench does not help with the outputs
- **initial** statement is similar to **always**, it just starts once at the beginning, and does not repeat.
- The statements have to be blocking.

Self-checking Testbench

```
module testbench2();
  reg  a, b, c;
  wire y;

  // instantiate device under test
  sillyfunction dut(.a(a), .b(b), .c(c), .y(y));

  // apply inputs one at a time
  initial begin
    a = 0; b = 0; c = 0; #10; // apply input, wait
    if (y !== 1) $display("000 failed."); // check
    c = 1; #10; // apply input, wait
    if (y !== 0) $display("001 failed."); // check
    b = 1; c = 0; #10; // etc.. etc..
    if (y !== 0) $display("010 failed."); // check
  end
endmodule
```


Self-checking Testbench

- Better than simple testbench
- This testbench also includes a statement to check the current state
- `$display` will write a message in the simulator
- This is a lot of work
 - Imagine a 32-bit processor executing a program (thousands of clock cycles)
- You make the same amount of mistakes when writing testbenches as you do writing actual code

Testbench with Testvectors

- **The more elaborate testbench**
- **Write testvector file: inputs and expected outputs**
 - Usually can use a high-level model (golden model) to produce the 'correct' input output vectors
- **Testbench:**
 - Generate clock for assigning inputs, reading outputs
 - Read testvectors file into array
 - Assign inputs, get expected outputs from DUT
 - Compare outputs to expected outputs and report errors

Testbench with Testvectors

 

- **A testbench clock is used to synchronize I/O**
 - The same clock can be used for the DUT clock
- **Inputs are applied following a hold margin**
- **Outputs are sampled before the next clock edge**
 - The example in book uses the falling clock edge to sample

Testvectors File

- We need to generate a testvector file (somehow)
- File: `example.tv` – contains vectors of `abc_yexpected`

`000_1`

`001_0`

`010_0`

`011_0`

`100_1`

`101_1`

`110_0`

`111_0`

Testbench: 1. Generate Clock

```
module testbench3();
  reg          clk, reset;    // clock and reset are internal
  reg          a, b, c, yexpected; // values from testvectors
  wire         y;             // output of circuit
  reg [31:0] vectornum, errors; // bookkeeping variables
  reg [3:0] testvectors[10000:0]; // array of testvectors

  // instantiate device under test
  sillyfunction dut(.a(a), .b(b), .c(c), .y(y) );

  // generate clock
  always        // no sensitivity list, so it always executes
  begin
    clk = 1; #5; clk = 0; #5;      // 10ns period
  end
```

2. Read Testvectors into Array

```
// at start of test, load vectors
// and pulse reset

initial                // Will execute at the beginning once
begin
    $readmemb("example.tv", testvectors); // Read vectors
    vectornum = 0; errors = 0;             // Initialize
    reset = 1; #27; reset = 0;            // Apply reset wait
end

// Note: $readmemb reads testvector files written in
// hexadecimal
```

3. Assign Inputs and Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```

- Apply inputs with some delay (1ns) AFTER clock
- This is important
 - Inputs should not change at the same time with clock
- Ideal circuits (HDL code) are immune, but real circuits (netlists) may suffer from hold violations.

4. Compare Outputs with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset)                      // skip during reset
    begin
      if (y !== yexpected)
        begin
          $display("Error: inputs = %b", {a, b, c});
          $display("  outputs = %b (%b exp)", y, yexpected);
          errors = errors + 1;
        end
    end
// Note: to print in hexadecimal, use %h. For example,
//       $display("Error: inputs = %h", {a, b, c});
```

4. Compare Outputs with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx)
begin
    $display("%d tests completed with %d errors",
            vectornum, errors);
    $finish;                // End simulation
end
end
endmodule

// Note: === and !== can compare values that are
// x or z.
```

Golden Models

- **A golden model represents the ideal behavior of your circuit.**
 - Still it has to be developed
 - It is difficult to get it right (bugs in the golden model!)
 - Can be done in C, Perl, Python, Matlab or even in Verilog
- **The behavior of the circuit is compared against this golden model.**
 - Allows automated systems (very important)

Why is Verification difficult?

■ How long would it take to test a 32-bit adder?

- In such an adder there are 64 inputs = 2^{64} possible inputs
- That makes around $1.85 \cdot 10^{19}$ possibilities
- If you test one input in 1ns, you can test 10^9 inputs per second
 - or 8.64×10^{14} inputs per day
 - or 3.15×10^{17} inputs per year
- we would still need **58.5 years** to test all possibilities

■ Brute force testing is not feasible for all circuits, we need alternatives

- Formal verification methods
- Choosing 'critical cases'
- Not an easy task